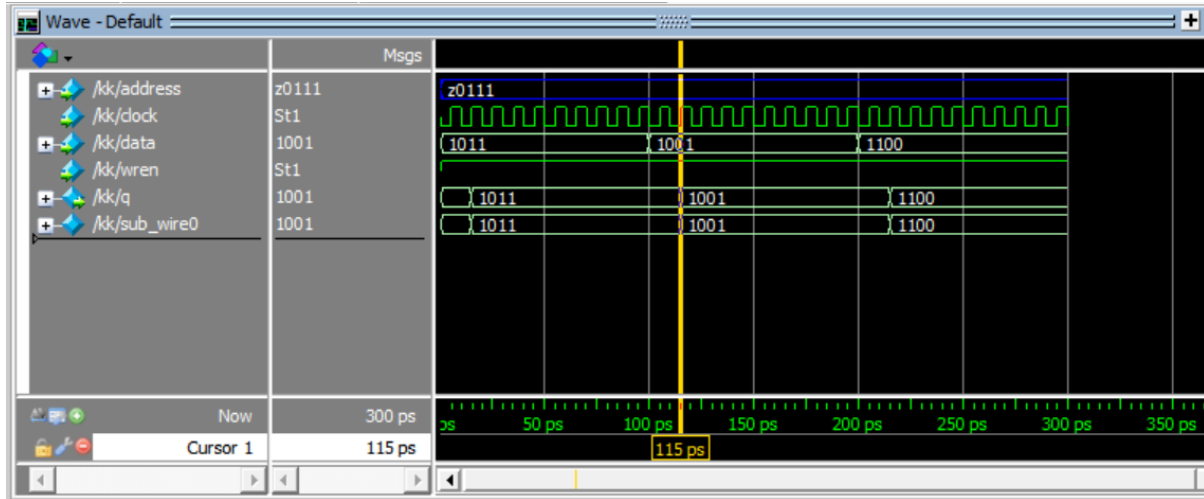


Prelab for Lab7

Xiaoyu Zhou, 1004081147

Part I

9. Simulation



10. Instantiate the ram32x4 module into a top-level Verilog modul

```
module top (SW, KEY, HEX0, HEX2, HEX4, HEX5);
    input [9:0] SW;
    input [3:0] KEY;
    output [6:0] HEX0;
    output [6:0] HEX2;
    output [6:0] HEX4;
    output [6:0] HEX5;
    wire out;

    kk u1(
        .address(SW[8:4]),
        .clock(KEY[0]),
        .data(SW[3:0]),
        .wren(SW[9]),
        .q(out)
    );

    hex dataa(
        .in2(SW[3]),
        .in3(SW[2]),
        .in4(SW[1]),
        .in5(SW[0]),
        .o2(HEX2[0]),
        .o3(HEX2[1]),
        .o4(HEX2[2]),
        .o5(HEX2[3]),
        .o6(HEX2[4]),
        .o7(HEX2[5]),
        .o8(HEX2[6])
    );

    hex outtt(
        .in2(out[3]),
        .in3(out[2]),
        .in4(out[1]),
        .in5(out[0]),
        .o2(HEX0[0]),
        .o3(HEX0[1]),
        .o4(HEX0[2]),
        .o5(HEX0[3]),
        .o6(HEX0[4])
    );
endmodule
```

```

        .o7(HEX0[5]),
        .o8(HEX0[6])
    );

    hex addd1(
        .in2(SW[7]),
        .in3(SW[6]),
        .in4(SW[5]),
        .in5(SW[4]),
        .o2(HEX4[0]),
        .o3(HEX4[1]),
        .o4(HEX4[2]),
        .o5(HEX4[3]),
        .o6(HEX4[4]),
        .o7(HEX4[5]),
        .o8(HEX4[6])
    );

    hex addd2(
        .in2(0),
        .in3(0),
        .in4(0),
        .in5(SW[8]),
        .o2(HEX5[0]),
        .o3(HEX5[1]),
        .o4(HEX5[2]),
        .o5(HEX5[3]),
        .o6(HEX5[4]),
        .o7(HEX5[5]),
        .o8(HEX5[6]),
        .o7(HEX5[5]),
        .o8(HEX5[6])
    );

endmodule

// synopsys translate_off
`timescale 1 ps / 1 ps
// synopsys translate_on
module kk (
    address,
    clock,
    data,
    wren,
    q);

    input [4:0] address;
    input clock;
    input [3:0] data;
    input wren;
    output [3:0] q;
`ifndef ALTERA_RESERVED_QIS
// synopsys translate_off
`endif
    tri0 clock;
`ifndef ALTERA_RESERVED_QIS
// synopsys translate_on
`endif

    wire [3:0] sub_wire0;
    wire [3:0] q = sub_wire0[3:0];

    altsyncram altsyncram_component (
        .address_a (address),
        .clock0 (clock),
        .data_a (data),
        .wren_a (wren),
        .q_a (sub_wire0),
        .aclr0 (1'b0),
        .aclr1 (1'b0),
        .address_b (1'b1),
        .addressstall_a (1'b0),
        .addressstall_b (1'b0),
        .byteena_a (1'b1),
        .byteena_b (1'b1),
        .clock1 (1'b1),
        .clocken0 (1'b1),
        .clocken1 (1'b1),
        .clocken2 (1'b1),
        .clocken3 (1'b1),
        .data_b (1'b1),
        .eccstatus (),
        .q_b (),
        .rden_a (1'b1),
        .rden_b (1'b1),
        .wren_b (1'b0));

    defparam
        altsyncram_component.clock_enable_input_a = "BYPASS",
        altsyncram_component.clock_enable_output_a = "BYPASS",
        altsyncram_component.intended_device_family = "Cyclone V",

```

```

        altsyncram_component.lpm_hint = "ENABLE_RUNTIME_MOD=NO",
        altsyncram_component.lpm_type = "altsyncram",
        altsyncram_component.numwords_a = 32,
        altsyncram_component.operation_mode = "SINGLE_PORT",
        altsyncram_component.outdata_aclr_a = "NONE",
        altsyncram_component.outdata_reg_a = "CLOCK0",
        altsyncram_component.power_up_uninitialized = "FALSE",
        altsyncram_component.read_during_write_mode_port_a = "NEW_DATA_NO_NBE_READ",
        altsyncram_component.width_a = 5,
        altsyncram_component.width_a = 4,
        altsyncram_component.width_byteena_a = 1;

endmodule

module hex(in2, in3, in4, in5, o2, o3, o4, o5, o6, o7, o8);
    input in2;
    input in3;
    input in4;
    input in5;
    output o2;
    output o3;
    output o4;
    output o5;
    output o6;
    output o7;
    output o8;

    hex0 u1(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out1(o2)
    );

    hex1 u2(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out2(o3)
    );

    hex2 u3(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out3(o4)
    );

    hex3 u4(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out4(o5)
    );

    hex4 u5(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out5(o6)
    );

    hex5 u6(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out6(o7)
    );

    hex6 u7(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out7(o8)
    );
endmodule

module hex0(c3, c2, c1, c0, out1);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out1; //output

```

```

    assign out1 = ~c3 & c2 & ~c1 & ~c0 | c3 & c2 & ~c1 & c0 | c3 & ~c2 & c1 & c0 | ~c3 & ~c2 & ~c1 & c0;
endmodule

module hex1(c3, c2, c1, c0, out2);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out2; //output

    assign out2 = c2 & c1 & ~c0 | c3 & c1 & c0 | ~c3 & c2 & ~c1 & c0 | c3 & c2 & ~c0;
endmodule

module hex2(c3, c2, c1, c0, out3);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out3; //output

    assign out3 = ~c3 & ~c2 & c1 & ~c0 | c3 & c2 & c1 | c3 & c2 & ~c0;
endmodule

module hex3(c3, c2, c1, c0, out4);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out4; //output

    assign out4 = ~c3 & c2 & ~c1 & ~c0 | ~c2 & ~c1 & c0 | c2 & c1 & c0 | c3 & ~c2 & c1 & ~c0;
endmodule

module hex4(c3, c2, c1, c0, out5);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out5; //output
    assign out5 = ~c3 & c2 & ~c1 | ~c2 & ~c1 & c0 | ~c3 & c0;
endmodule

module hex5(c3, c2, c1, c0, out6);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out6; //output


    assign out6 = ~c3 & ~c2 & c0 | ~c3 & ~c2 & c1 | ~c3 & c1 & c0 | c3 & c2 & ~c1 & c0;
endmodule

module hex6(c3, c2, c1, c0, out7);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out7; //output

    assign out7 = ~c3 & ~c2 & ~c1 | c3 & c2 & ~c1 & ~c0 | ~c3 & c2 & c1 & c0;
endmodule

```

11. Schematic.

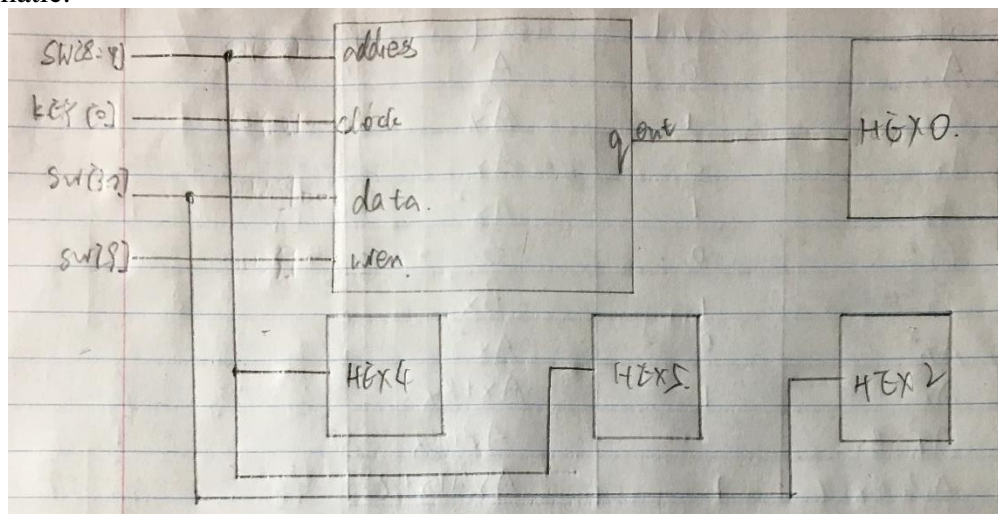

Part II

1. Verilog:

```
module datapath(clk, temp_x, temp_y, temp_c, reset_n, go, color_in, position, x_out, y_out, color_out);

    input clk, temp_x, temp_y, temp_c, reset_n, go;
    input [2:0] color_in;
    input [6:0] position;

    output [7:0] x_out;
    output [6:0] y_out;
    output [2:0] color_out;

    reg [2:0] count_x, count_y;
    reg [7:0] real_x;
    reg [6:0] real_y;
    reg [2:0] color;

    // registers for x, y and color
    always @(posedge clk) begin
        if (!reset_n) begin
            real_x <= 8'b0;
            real_y <= 7'b0;
            color <= 3'b0;
        end
        else begin
            if (temp_x)
                real_x <= {1'b0, position};
            if (temp_y)
                real_y <= position;
            if (temp_c)
                color <= color_in;
        end
    end


    // counter for x
    always @(posedge clk) begin
        if (!reset_n)
            count_x <= 2'b00;
        else if (go) begin
            if (count_x == 2'b11)
                count_x <= 2'b00;
            else begin
                count_x <= count_x + 1'b1;
            end
        end
    end

    // counter for y
    always @(posedge clk) begin
        if (!reset_n)
            count_y <= 2'b00;
        else if (go && (count_x == 2'b11)) begin
            if (count_y != 2'b11)
                count_y <= count_y + 1'b1;
            else
                count_y <= 2'b00;
        end
    end

    assign x_out = real_x + count_x;
    assign y_out = real_y + count_y;
    assign color_out = color;


endmodule
```

Simulation:

 

2.

State Diagram

 

State Table

State		Next State
X	0	X
X	1	Y
Y	0	Y
Y	1	C
C	0	C
C	1	X

Verilog

```

module control(clk, reset_n, ld, draw, temp_x, temp_y, temp_c, go);
    input clk, reset_n, ld, draw;
    output reg temp_x, temp_y, temp_c, go;
    reg [2:0] current_state, next_state;

    localparam
        Load_x = 3'd0,
        Load_x_wait = 3'd1,
        Load_y = 3'd2,
        Load_y_wait = 3'd3,
        Load_c = 3'd4,
        Load_c_wait = 3'd5,
        Draw = 3'd6;

    always @(*) begin
        case (current_state)
            Load_x: next_state = ld ? Load_x_wait : Load_x;
            Load_x_wait: next_state = ld ? Load_x_wait : Load_y;
            Load_y: next_state = ld ? Load_y_wait : Load_y;
            Load_y_wait: next_state = ld ? Load_y_wait : Load_c;
        end
    end
endmodule

```

```

        Load_c: next_state = draw ? Load_c_wait : Load_c;
        Load_c_wait: next_state = draw ? Load_c_wait : Draw;
        Draw: next_state = ld ? Load_x : Draw;
    endcase
end


always @(*) begin
    temp_x = 1'b0;
    temp_y = 1'b0;
    temp_c = 1'b0;
    go = 1'b0;

    case (current_state)
        Load_x: begin
            temp_x = 1;
        end
        Load_y: begin
            temp_y = 1;
        end
        Load_c: begin
            temp_c = 1;
        end
        Draw: begin
            go = 1;
        end
    endcase
end


always @(posedge clk) begin
    if (!reset_n)
        current_state <= Load_x;
    else
        current_state <= next_state;
    end
end
endmodule

```

Simulation

 

3. Simulation

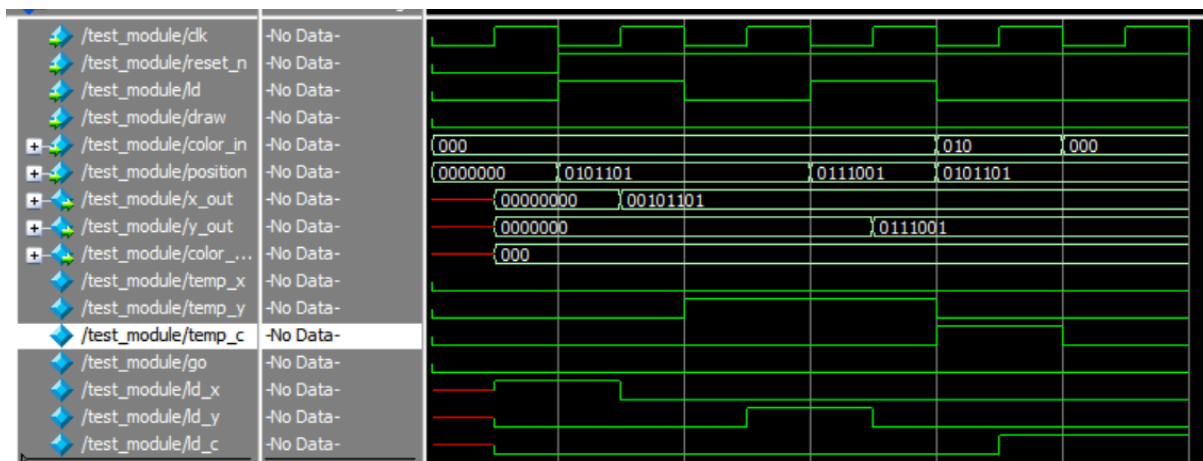

Part III

Verilog

```
module datapath(enable,clock,ld_c,colour,reset_n,X,Y,colour_out);
    input enable,clock,reset_n,ld_c;
    input [2:0] colour;
    output[7:0] X,Y;
    output[2:0] colour_out;

    wire enable_fc;
    wire enable_xy;
    wire[3:0] c1;
    wire signal_x,signal_y;
    wire[7:0] x_in,y_in;
    wire[2:0] colour_1;

    x_counter x_c(
        .x_in(x_in),
        .clock(clock),
        .reset_n(reset_n),
        .enable(enable_xy),
        .x_out(x_in)
    );


    y_counter y_c(
        .y_in(y_in),
        .clock(clock),
        .reset_n(reset_n),
        .enable(enable_xy),
        .y_out(y_in)
    );

    delay_counter dc1(
        .clock(clock),
        .reset_n(reset_n),
        .enable(enable),
        .enable_fc(enable_fc)
    );

    frame_counter fc2(
        .clock(clock),
        .reset_n(reset_n),
        .enable(enable_fc),
        .enable_xy(enable_xy),
        .colour_1(colour_1),
        .colour(colour)
    );


    draw dr1(x_in,y_in,colour_1,ld_c,clock,reset_n,enable,X,Y,colour_out);
endmodule
```

Simulation

 

2.

State Diagram

 

Verilog

```
module control(clock,reset_n,go,enable,ld_c,plot);
    input clock,reset_n,go;
    output reg enable,ld_c,plot;

    reg [3:0] current_state, next_state;

    localparam S_LOAD_C          = 4'd0,
               S_LOAD_C_WAIT    = 4'd1,
               S_CYCLE_0        = 4'd2;

    always@(*)
    begin: state_table
        case (current_state)
            S_LOAD_C: next_state = go ? S_LOAD_C_WAIT : S_LOAD_C;
            S_LOAD_C_WAIT: next_state = go ? S_LOAD_C_WAIT : S_CYCLE_0;
            S_CYCLE_0: next_state = S_CYCLE_0;
            default:    next_state = S_LOAD_C;
        endcase
    end

    always@(*)
    begin: enable_signals
        // By default make all our signals 0
        ld_c = 1'b0;
        enable = 1'b0;
        plot = 1'b0;

        case(current_state)
            S_LOAD_C:begin
                end
            S_CYCLE_0:begin
                ld_c = 1'b1;
                enable = 1'b1;
                plot = 1'b1;
            end
        endcase
    end

    always@(posedge clock)
    begin: state_FF
        if(!reset_n)
            current_state <= S_LOAD_C;
        else
            current_state <= next_state;
        end
    end
endmodule
```

Simulation

