 


Prelab for Lab5

Xiaoyu Zhou, 1004081147

Part I

1.2. The schematic



3. Write the Verilog

```
module mux(SW, KEY, HEX0, HEX1);
    wire [7:0] Q;
    input [1:0] SW;
    input [2:0] KEY;
    output [6:0] HEX0;
    output [6:0] HEX1;

    counter a(
        .enable(SW[1]),
        .clock(KEY[0]),
        .clearb(SW[0]),
        .Q(Q[7:0])
    );

    hex u0(
        .in2(Q[3]),
        .in3(Q[2]),
        .in4(Q[1]),
        .in5(Q[0]),
        .o2(HEX0[0]),
        .o3(HEX0[1]),
        .o4(HEX0[2]),
        .o5(HEX0[3]),
        .o6(HEX0[4]),
        .o7(HEX0[5]),
        .o8(HEX0[6])
    );

    hex u1(
        .in2(Q[7]),
        .in3(Q[6]),
        .in4(Q[5]),
        .in5(Q[4]),
        .o2(HEX1[0]),
        .o3(HEX1[1]),
        .o4(HEX1[2]),
        .o5(HEX1[3]),
        .o6(HEX1[4]),
        .o7(HEX1[5]),
        .o8(HEX1[6])
    );
endmodule

module counter(enable, clock, clearb, Q);
    input enable;
    input clock;
    input clearb;
    output [7:0] Q;
    wire in1, in2, in3, in4, in5, in6, in7, in8;

    T_flipflop a(
        .T(enable),
        .clock(clock),
        .c(clearb),
        .Q(Q[7])
    );

    assign in1 = enable & Q[7];

    T_flipflop b(
        .T(in1),
        .clock(clock),
        .c(clearb),
        .Q(Q[6])
    );

    assign in2 = in1 & Q[6];

    T_flipflop c(
        .T(in2),
        .clock(clock),
        .c(clearb),
        .Q(Q[5])
    );

    assign in3 = in2 & Q[5];

    T_flipflop d(
        .T(in3),
        .clock(clock),
        .c(clearb),
        .Q(Q[4])
    );

    assign in4 = in3 & Q[4];

    T_flipflop e(
        .T(in4),
        .clock(clock),
        .c(clearb),
        .Q(Q[3])
    );

    assign in5 = in4 & Q[3];

    T_flipflop f(
        .T(in5),
        .clock(clock),
        .c(clearb),
        .Q(Q[2])
    );

    assign in6 = in5 & Q[2];

    T_flipflop g(
        .T(in6),
        .clock(clock),
        .c(clearb),
        .Q(Q[1])
    );

    assign in7 = in6 & Q[1];

    T_flipflop h(
        .T(in7),
        .clock(clock),
        .c(clearb),
        .Q(Q[0])
    );

    assign in8 = in7 & Q[0];
endmodule
```

```

        );

    assign in7 = in6 & Q[1];

    T_flipflop h(
        .T(in7),
        .clock(clock),
        .c(clearb),
        .Q(Q[0])
    );
endmodule

module T_flipflop(T, clock, c, Q);
    parameter N = 1;
    input T;
    input [N-1:0] clock;
    input [N-1:0] c;
    output Q;
    wire connect;

    assign connect = T ^ Q;

    D_flipflop dd(
        .d(connect),
        .clock(clock),
        .reset_n(c),
        .q(Q)
    );
endmodule

module D_flipflop(d, clock, reset_n, q);
    parameter N = 1;
    input d;
    input [N-1:0] clock;
    input [N-1:0] reset_n;
    output q;
    reg q;

    always @(posedge clock, negedge reset_n)
    begin
        if (reset_n == 1'b0)
            q <= 0;
        else
            q <= d;
        end
    end
endmodule

module hex(in2, in3, in4, in5, o2, o3, o4, o5, o6, o7, o8);
    input in2;
    input in3;
    input in4;
    input in5;
    output o2;
    output o3;
    output o4;
    output o5;
    output o6;
    output o7;
    output o8;

    hex0 u1(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out1(o2)
    );

    hex1 u2(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out2(o3)
    );

    hex2 u3(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out3(o4)
    );

    hex3 u4(
        .c3(in2),
        .c2(in3),

```

```

        .c1(in4),
        .c0(in5),
        .out4(o5)
    );

    hex4 u5(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out5(o6)
    );

    hex5 u6(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out6(o7)
    );

    hex6 u7(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out7(o8)
    );
endmodule

module hex0(c3, c2, c1, c0, out1);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out1; //output

    assign out1 = ~c3 & c2 & ~c1 & ~c0 | c3 & c2 & ~c1 & c0 |
    c3 & ~c2 & c1 & c0 | ~c3 & ~c2 & ~c1 & c0;
endmodule

module hex1(c3, c2, c1, c0, out2);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out2; //output

    assign out2 = c2 & c1 & ~c0 | c3 & c1 & c0 | ~c3 & c2 & ~c1
    & c0 | c3 & c2 & ~c0;
endmodule

module hex2(c3, c2, c1, c0, out3);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out3; //output

    assign out3 = ~c3 & ~c2 & c1 & ~c0 | c3 & c2 & c1 | c3 & c2
    & ~c0;
endmodule

module hex3(c3, c2, c1, c0, out4);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out4; //output

    assign out4 = ~c3 & c2 & ~c1 & ~c0 | ~c2 & ~c1 & c0 | c2 &
    c1 & c0 | c3 & ~c2 & c1 & ~c0;
endmodule

module hex4(c3, c2, c1, c0, out5);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out5; //output

    assign out5 = ~c3 & c2 & ~c1 | ~c2 & ~c1 & c0 | ~c3 & c0;

```

endmodule

```
module hex5(c3, c2, c1, c0, out6);
  input c3; //selected when s is 0
  input c2; //selected when s is 1
  input c1; //select signal
  input c0;
  output out6; //output
```

```
  assign out6 = ~c3 & ~c2 & c0 | ~c3 & ~c2 & c1 | ~c3 & c1 &
c0 | c3 & c2 & ~c1 & c0;
```


endmodule

```
module hex6(c3, c2, c1, c0, out7);
  input c3; //selected when s is 0
  input c2; //selected when s is 1
  input c1; //select signal
  input c0;
  output out7; //output
```


```
  assign out7 = ~c3 & ~c2 & ~c1 | c3 & c2 & ~c1 & ~c0 | ~c3
& c2 & c1 & c0;
```

endmodule

4. Simulate first.

 

 5. Simulate second time, with connect to the switches.




6.(1) The percentage of FPGA logic resources are used is less than 1%.

Quartus Prime Version	18.0.0 Build 614 04/24/2018 SJ Lite Edition
Revision Name	mux
Top-level Entity Name	mux
Family	Cyclone V
Device	5CSEMA5F31C6
Timing Models	Final
Logic utilization (in ALMs)	13 / 32,070 (< 1 %)
Total registers	8
Total pins	19 / 457 (4 %)
Total virtual pins	0
Total block memory bits	0 / 4,065,280 (0 %)
Total RAM Blocks	0 / 397 (0 %)
Total DSP Blocks	0 / 87 (0 %)
Total HSSI RX PCSs	0
Total HSSI PMA RX Deserializers	0
Total HSSI TX PCSs	0
Total HSSI PMA TX Serializers	0
Total PLLs	0 / 6 (0 %)
Total DLLs	0 / 4 (0 %)

(2) The maximum clock frequency, F_{\max} is 621.89 MHz..

	Fmax	Restricted Fmax	Clock Name	Note
1	654.02 MHz	621.89 MHz	KEY[0]	limit due to low minimum pulse width violation (tcl)

7. The schematic of RTL viewer looks much more complex. And it puts all T-flipflops together instead of putting them in order.

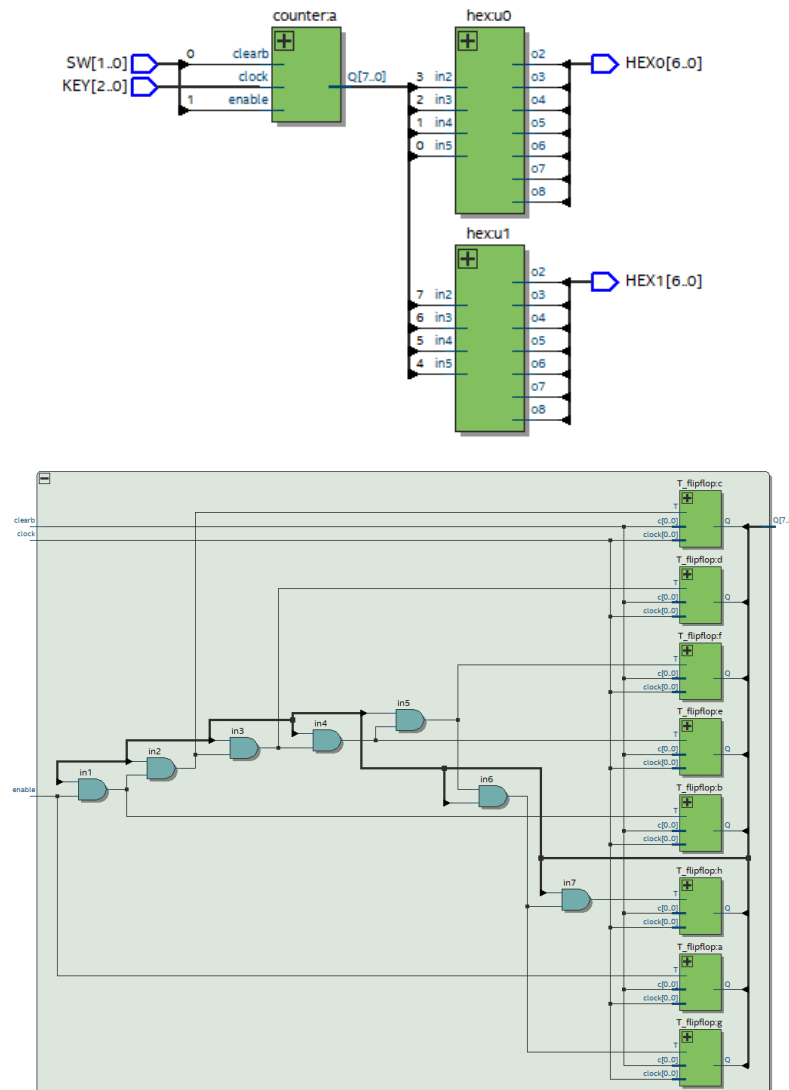

Part II

Q1: In this implementation, q is declared as a 4-bit value, which makes this a 4-bit counter.

The check for the maximum value is not necessary in the example above. Why?

A: Since the range of this implementation is from 0 to F, which is also the range for the 4-bits.

Q2: If you wanted this 4-bit counter to count from 0-9, what would you change?

A: Change the if statement 'q == 4'b1111' into 'q == 4'b1001'.


Q3: Full speed means that the display flashes at the rate of the 50 MHz clock provided on the DE1-SoC board. At this speed, what do you expect to see on the display?

A: The period will be 20ns. So, the flashes will be the same as the clock changes.

Q4: How large a counter is required to count 50 million clock cycles? A: 50 million.

Q5: How many bits would you need to represent such a value? A: 25 bits

1. Draw a schematic.

 

2. Write a Verilog module.

```

module mux(SW, KEY, CLOCK_50, HEX0);
    input [1:0] SW;
    input [2:0] KEY;
    input CLOCK_50;
    output [6:0] HEX0;
    wire connect;
    wire [3:0] Q;

    RateDivider a(
        .m(SW[1]),
        .n(SW[0]),
        .clock(CLOCK_50),
        .out(connect)
    );

    DisplayCounter b(
        .enable(connect),
        .reset_n(KEY[0]),
        .clock2(CLOCK_50),
        .q(Q[3:0])
    );

    hex u0(
        .in2(Q[3]),
        .in3(Q[2]),
        .in4(Q[1]),
        .in5(Q[0]),
        .o2(HEX0[0]),
        .o3(HEX0[1]),
        .o4(HEX0[2]),
        .o5(HEX0[3]),
        .o6(HEX0[4]),
        .o7(HEX0[5]),
        .o8(HEX0[6])
    );
endmodule

module RateDivider(m, n, clock, out);
    parameter N = 28;
    input m, n;
    input clock;
    output out;
    reg [N-1:0] count;
    reg out;

    always @(posedge clock)
    begin
        if (m == 0)
            begin
                if (n == 0)
                    assign count = clock;
                else if (n == 1)
                    begin
                        if (count ==
                            28'b0010111101010111000001111111)
                            count <= 0;
                        else
                            count <= count +
                                1'b1;
                    end
                end
            end
    end

```

```

        else if (m == 1)
            begin
                if (n == 0)
                    begin
                        if (count ==
28'b0101111101011110000011111111)
                            count
<= 0;
                        else
                            count
<= count + 1'b1;
                    end
                else if (n == 1)
                    begin
                        if (count ==
28'b1011111101011110000011111111)
                            count
<= 0;
                        else
                            count
<= count + 1'b1;
                    end
            end
        if (count == 0)
            out <= 1;
        else
            out <= 0;
    end
endmodule

module DisplayCounter(enable, reset_n, clock2, q);
    parameter k = 4;
    input enable, reset_n, clock2;
    output [k-1:0] q;
    reg [k-1:0] q;

    always @(posedge clock2)
        begin
            if (reset_n == 1'b0)
                q <= 0;
            else if (enable == 1'b1)
                begin
                    if (q == 4'b1111)
                        q <= 0;
                    else
                        q <= q + 1'b1;
                end
        end
    end
endmodule

module hex(in2, in3, in4, in5, o2, o3, o4, o5, o6, o7, o8);
    input in2;
    input in3;
    input in4;
    input in5;
    output o2;
    output o3;
    output o4;
    output o5;
    output o6;
    output o7;
    output o8;

    hex0 u1(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out1(o2)
    );

    hex1 u2(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out2(o3)
    );

    hex2 u3(
        .c3(in2),

```

```

        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out3(o4)
    );

    hex3 u4(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out4(o5)
    );

    hex4 u5(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out5(o6)
    );

    hex5 u6(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out6(o7)
    );

    hex6 u7(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out7(o8)
    );
endmodule

module hex0(c3, c2, c1, c0, out1);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out1; //output

    assign out1 = ~c3 & c2 & ~c1 & ~c0 | c3 & c2 & ~c1 & c0 |
c3 & ~c2 & c1 & c0 | ~c3 & ~c2 & ~c1 & c0;
endmodule

module hex1(c3, c2, c1, c0, out2);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out2; //output

    assign out2 = c2 & c1 & ~c0 | c3 & c1 & c0 | ~c3 & c2 & ~c1
& c0 | c3 & c2 & ~c0;
endmodule

module hex2(c3, c2, c1, c0, out3);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out3; //output

    assign out3 = ~c3 & ~c2 & c1 & ~c0 | c3 & c2 & c1 | c3 & c2
& ~c0;
endmodule

module hex3(c3, c2, c1, c0, out4);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out4; //output

    assign out4 = ~c3 & c2 & ~c1 & ~c0 | ~c2 & ~c1 & c0 | c2 &
c1 & c0 | c3 & ~c2 & c1 & ~c0;
endmodule

```

```

module hex4(c3, c2, c1, c0, out5);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out5; //output

    assign out5 = ~c3 & c2 & ~c1 | ~c2 & ~c1 & c0 | ~c3 & c0;
endmodule

module hex5(c3, c2, c1, c0, out6);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out6; //output


    assign out6 = ~c3 & ~c2 & c0 | ~c3 & ~c2 & c1 | ~c3 & c1 &
c0 | c3 & c2 & ~c1 & c0;
endmodule

module hex6(c3, c2, c1, c0, out7);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out7; //output

    assign out7 = ~c3 & ~c2 & ~c1 | c3 & c2 & ~c1 & ~c0 | ~c3
& c2 & c1 & c0;
endmodule

```

3. Simulation.

 


Part III

1. Use Table 1 to determine your code and bit-width.

Letter	Pattern Representation (pattern length is 11 bits)
A	10111000000
B	11101010100
C	11101011101
D	11101010000
E	10000000000
F	10101110100
G	11101110100

H	10101010000
---	-------------

2. Draw a schematic.

 

3. Write a Verilog module.

```
module mux(SW, KEY, CLOCK_50, LEDR);
    input [2:0] SW;
    input [2:0] KEY;
    input CLOCK_50;
    output [1:0] LEDR;
    wire connect;
    wire [11:0] Q;
```

```
    RateDivider a(
        .clock(CLOCK_50),
        .out(connect)
    );
```

```
    DisplayCounter b(
        .enable(connect),
        .reset_n(KEY[0]),
        .in(q[11:0]),
        .start(KEY[1]),
        .clock2(CLOCK_50),
        .L(LEDR[0])
    );
```

```
    LUT c(
        .m(SW[2]),
        .n(SW[1]),
        .o(SW[0]),
        .outt(Q[11:0])
    );
```

```
endmodule
```

```
module RateDivider(clock, out);
    parameter N = 25;
    input clock;
    output out;
    reg [N-1:0] count;
    reg out;

    always @(posedge clock)
    begin
        if (count == 25'b1011111010111100001000000)
            count <= 0;
        else
            count <= count + 1'b1;

        if (count == 0)
            out <= 1;
        else
            out <= 0;
    end
endmodule
```

```
module ShiftRegister(enable, reset_n, in, start, clock2, L);
    parameter k = 11;
    parameter s = 3;
    input enable, reset_n, start, clock2;
    input [k-1:0] in;
```

```
    output L;
    wire [s-1:0] q;

    always @(posedge clock2, posedge reset_n)
    begin
        if (reset_n == 1'b0)
            q <= 0;
        else if (start == 1'b1)
            q <= 0;
        else if (enable == 1'b1)
            begin
                if (q == 4'b1111)
                    q <= 0;
                else
                    q <= q + 1'b1;
            end
    end
```

```
    always @(posedge clock2, posedge reset_n)
    begin
        case(q)
            4'b0000: L = 0;
            4'b0001: L = in[10];
            4'b0010: L = in[9];
            4'b0011: L = in[8];
            4'b0100: L = in[7];
            4'b0101: L = in[6];
            4'b0110: L = in[5];
            4'b0111: L = in[4];
            4'b1000: L = in[3];
            4'b1001: L = in[2];
            4'b1010: L = in[1];
            4'b1011: L = in[0];
            default: L = 0;
        endcase
    end
endmodule
```

```
module LUT(m, n, o, outt);
    parameter a = 11;
    input m, n, o;
    output [a-1:0] outt;

    always @(*)
    begin
        case(in1)
            3'b000: outt = 11'b101110000000;
            3'b001: outt = 11'b11101010100;
            3'b010: outt = 11'b11101011101;
            3'b011: outt = 11'b11101010000;
            3'b100: outt = 11'b10000000000;
            3'b101: outt = 11'b10101110100;
            3'b110: outt = 11'b11101110100;
            3'b111: outt = 11'b10101010000;
            default: outt = 11'b0000_0000_000;
        endcase
    end
endmodule
```