

Prelab for Lab6

Xiaoyu Zhou, 1004081147

Part I

2. The **resetn** signal is a synchronous reset and it is active low. When I do the simulation, I need to begin with setting **resetn** to be 0.

3. Verilog Code:

```
// SW[0]:      reset signal
// SW[1]:      input signal (w)

// KEY[0]:     clock

// LEDR[2:0]:  current state
// LEDR[9]:    output (z)

module sequence_detector(SW, KEY, LEDR);
    input [9:0] SW;
    input [3:0] KEY;
    output [9:0] LEDR;

    wire w, clock, resetn, z;

    reg [2:0] y_Q, Y_D; // y_Q represents current state, Y_D represents next state

    localparam A = 3'b000, B = 3'b001, C = 3'b010, D = 3'b011, E = 3'b100, F = 3'b101, G = 3'b110;

    // Connect inputs and outputs to internal wires
    assign w = SW[1];
    assign clock = ~KEY[0];
    assign resetn = SW[0];
    assign LEDR[9] = z;
    assign LEDR[2:0] = y_Q;

    // State table
    // The state table should only contain the logic for state transitions
    // Do not mix in any output logic. The output logic should be handled separately.
    // This will make it easier to read, modify and debug the code.
    always @(*)
    begin // Start of state_table
        case (y_Q)
            A: begin
                if (!w) Y_D = A;
                else Y_D = B;
            end
            B: begin
                if (!w) Y_D = A;
                else Y_D = C;
            end
            C: begin
                if (!w) Y_D = E;
                else Y_D = D;
            end
            D: begin
                if (!w) Y_D = E;
                else Y_D = F;
            end
            E: begin
                if (!w) Y_D = A;
                else Y_D = G;
            end
            F: begin
                if (!w) Y_D = E;
                else Y_D = F;
            end
            G: begin
                if (!w) Y_D = A;
                else Y_D = C;
            end
            default: Y_D = A;
        endcase
    end
```

```


end      // End of state_table

// State Register (i.e., FFs)
always @(posedge clock)
begin    // Start of state_FF (state register)
    if(resetn == 1'b0)
        y_Q <= A;
    else
        y_Q <= Y_D;
end      // End of state_FF (state register)

// Output logic
// Set z to 1 to turn on LED when in relevant states
assign z = ((y_Q == F) || (y_Q == G)); // To be completed by you!
endmodule

```

4. Simulation.

 


Part II

2. Table

state	control	result
A	0	A
A	1	Ax
Ax	0	Ax
Ax	1	Ax^2
B	0	B
B	1	Bx
Ax^2	0	Ax^2
Ax^2	1	$Ax^2 + Bx$
$Ax^2 + Bx$	0	$Ax^2 + Bx$
$Ax^2 + Bx$	1	$Ax^2 + Bx + C$

3. State

 

4. Verilog

```

module control(
    input clk,
    input resetn,
    input go,

    output reg ld_a, ld_b, ld_c, ld_x, ld_r,
    output reg ld_alu_out,
    output reg [1:0] alu_select_a, alu_select_b,
    output reg alu_op
);

reg [3:0] current_state, next_state;

localparam S_LOAD_A = 4'd0,
           S_LOAD_A_WAIT = 4'd1,
           S_LOAD_B = 4'd2,
           S_LOAD_B_WAIT = 4'd3,
           S_LOAD_C = 4'd4,
           S_LOAD_C_WAIT = 4'd5,
           S_LOAD_X = 4'd6,
           S_LOAD_X_WAIT = 4'd7,
           S_CYCLE_0 = 4'd8,
           S_CYCLE_1 = 4'd9,
           S_CYCLE_2 = 4'd10,
           S_CYCLE_3 = 4'd11,
           S_CYCLE_4 = 4'd12;

// Next state logic aka our state table
always@(*)
begin: state_table
    case (current_state)
        S_LOAD_A: next_state = go ? S_LOAD_A_WAIT : S_LOAD_A; // Loop in current state until value is input
        S_LOAD_A_WAIT: next_state = go ? S_LOAD_A_WAIT : S_LOAD_B; // Loop in current state until go signal goes
    low
        S_LOAD_B: next_state = go ? S_LOAD_B_WAIT : S_LOAD_B; // Loop in current state until value is input
        S_LOAD_B_WAIT: next_state = go ? S_LOAD_B_WAIT : S_LOAD_C; // Loop in current state until go signal goes
    low
        S_LOAD_C: next_state = go ? S_LOAD_C_WAIT : S_LOAD_C; // Loop in current state until value is input
        S_LOAD_C_WAIT: next_state = go ? S_LOAD_C_WAIT : S_LOAD_X; // Loop in current state until go signal goes
    low
        S_LOAD_X: next_state = go ? S_LOAD_X_WAIT : S_LOAD_X; // Loop in current state until value is input
        S_LOAD_X_WAIT: next_state = go ? S_LOAD_X_WAIT : S_CYCLE_0; // Loop in current state until go signal goes
    low
        S_CYCLE_0: next_state = S_CYCLE_1;
        S_CYCLE_1: next_state = S_CYCLE_2;
        S_CYCLE_2: next_state = S_CYCLE_3;
        S_CYCLE_3: next_state = S_CYCLE_4;
        S_CYCLE_4: next_state = S_LOAD_A; // we will be done our two operations, start over after
    default: next_state = S_LOAD_A;
    endcase
end // state_table

// Output logic aka all of our datapath control signals
always @(*)
begin: enable_signals
    // By default make all our signals 0
    ld_alu_out = 1'b0;
    ld_a = 1'b0;
    ld_b = 1'b0;
    ld_c = 1'b0;
    ld_x = 1'b0;
    ld_r = 1'b0;
    alu_select_a = 2'b00;
    alu_select_b = 2'b00;
    alu_op = 1'b0;

    case (current_state)
        S_LOAD_A: begin
            ld_a = 1'b1;
        end
        S_LOAD_B: begin
            ld_b = 1'b1;
        end
        S_LOAD_C: begin
            ld_c = 1'b1;
        end
        S_LOAD_X: begin
            ld_x = 1'b1;
        end
        S_CYCLE_0: begin // Do A <- A * x
            ld_alu_out = 1'b1; ld_a = 1'b1; // store result back into A
            alu_select_a = 2'b00; // Select register A
        end
    endcase
end

```

```

        alu_select_b = 2'b11; // Also select register A
        alu_op = 1'b1; // Do multiply operation
    end

    S_CYCLE_1: begin // Do A <- Ax * x
        ld_alu_out = 1'b1; ld_a = 1'b1; // store result back into A
        alu_select_a = 2'b00; // Select register A
        alu_select_b = 2'b11; // Also select register A
        alu_op = 1'b1; // Do multiply operation
    end

    S_CYCLE_2: begin // Do B <- B * x
        ld_alu_out = 1'b1; ld_b = 1'b1; // store result back into B
        alu_select_a = 2'b01; // Select register B
        alu_select_b = 2'b11; // Also select register x
        alu_op = 1'b1; // Do multiply operation
    end

    S_CYCLE_3: begin // Do A <- Axx + Bx
        ld_alu_out = 1'b1; ld_a = 1'b1; // store result back into A
        alu_select_a = 2'b00; // Select register A
        alu_select_b = 2'b01; // Also select register B
        alu_op = 1'b0; // Do multiply operation
    end


    S_CYCLE_4: begin
        ld_r = 1'b1; // store result in result register
        alu_select_a = 2'b00; // Select register A
        alu_select_b = 2'b10; // Select register C
        alu_op = 1'b0; // Do Add operation
    end

    // default: // don't need default since we already made sure all of our outputs were assigned a value at the start of the always
endcase
end // enable_signals

// current_state registers
always@(posedge clk)
begin: state_FFs
    if(!resetrn)
        current_state <= S_LOAD_A;
    else
        current_state <= next_state;
    end // state_FFS
endmodule

```

5.

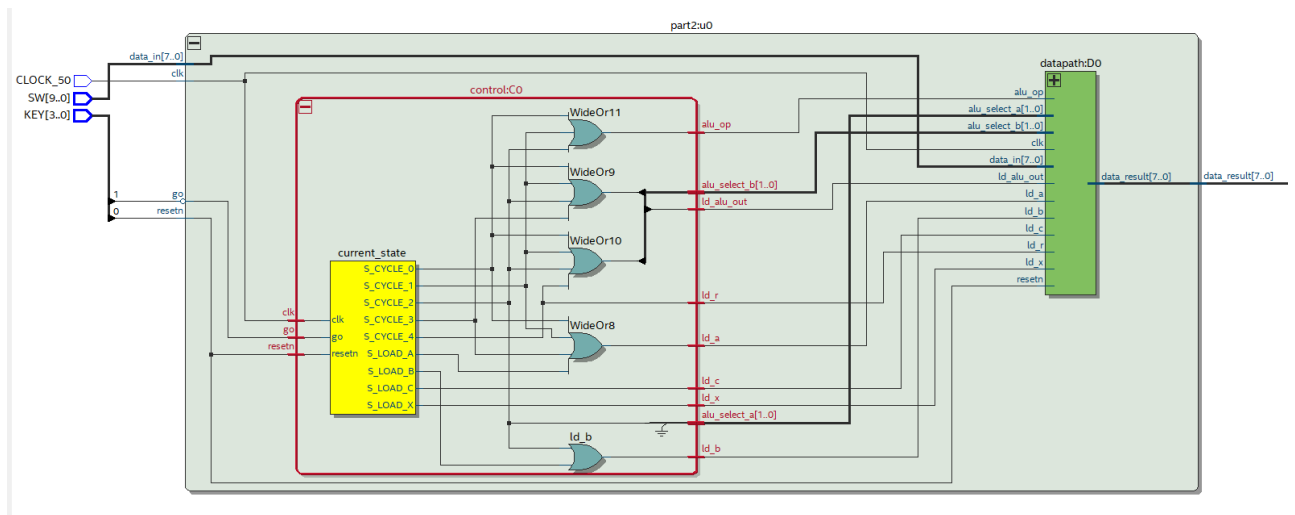

6. Simulation

