

Xiaoyu Zhou, 1004081147

Part I

-

HEX4, HEX5);

```

parameter Narrow = 4;
wire [Narrow-1:0] outt;
input [9:0] SW;
input [2:0] KEY;
output [9:0] LEDR;
output [6:0] HEX0;
output [6:0] HEX1;
output [6:0] HEX2;
output [6:0] HEX3;
output [6:0] HEX4;
output [6:0] HEX5;

```

```

trans u1(
    .A(SW[3:0]),
    .B(outt),
    .in1(SW[7:5]),
    .out1(LEDR[7:0])
);

```

```

D_flipflop a(
    .d(LEDR[3:0]),
    .clock(KEY[0]),
    .reset_n(SW[9]),
    .q(outt)
);

```

```

hex u2(
    .in2(LEDR[3]),
    .in3(LEDR[2]),
    .in4(LEDR[1]),
    .in5(LEDR[0]),
    .o2(HEX4[0]),
    .o3(HEX4[1]),
    .o4(HEX4[2]),
    .o5(HEX4[3]),
    .o6(HEX4[4]),
    .o7(HEX4[5]),
    .o8(HEX4[6])
);

```

```

hex u3(
    .in2(LEDR[7]),
    .in3(LEDR[6]),
    .in4(LEDR[5]),
    .in5(LEDR[4]),
    .o2(HEX5[0]),
    .o3(HEX5[1]),
    .o4(HEX5[2]),
    .o5(HEX5[3]),
    .o6(HEX5[4]),
    .o7(HEX5[5]),
    .o8(HEX5[6])
);

```

```

hex A(
    .in2(SW[3]),
    .in3(SW[2]),
    .in4(SW[1]),
    .in5(SW[0]),
    .o2(HEX0[0]),
    .o3(HEX0[1]),
    .o4(HEX0[2]),
    .o5(HEX0[3]),
    .o6(HEX0[4]),
    .o7(HEX0[5]),
    .o8(HEX0[6])
);

```

```

assign HEX1[6] = 1;
assign HEX1[5] = 1;
assign HEX1[4] = 1;
assign HEX1[3] = 1;
assign HEX1[2] = 1;
assign HEX1[1] = 1;
assign HEX1[0] = 1;

```

```

assign HEX2[6] = 1;
assign HEX2[5] = 1;
assign HEX2[4] = 1;
assign HEX2[3] = 1;
assign HEX2[2] = 1;
assign HEX2[1] = 1;
assign HEX2[0] = 1;

```

```

assign HEX3[6] = 1;
assign HEX3[5] = 1;
assign HEX3[4] = 1;
assign HEX3[3] = 1;
assign HEX3[2] = 1;
assign HEX3[1] = 1;
assign HEX3[0] = 1;

```

endmodule

```

module D_flipflop(d, clock, reset_n, q);
    parameter Narrow = 4;
    parameter N = 1;
    input [Narrow-1:0] d;
    input [N-1:0] clock;
    input [N-1:0] reset_n;
    output [Narrow-1:0] q;
    reg [Narrow-1:0] q;

```

```

    always @(posedge clock)
    begin
        if (reset_n == 1'b0)
            q <= 0;
        else
            q <= d;
    end
endmodule

```

endmodule

```

module trans(A, B, in1, out1);
    parameter Width = 8;
    parameter Narrow = 4;
    parameter W = 3;
    input [Narrow-1:0] A;
    input [Narrow-1:0] B;
    input [W-1:0] in1;
    output [Width-1:0] out1;
    reg [Width-1:0] out1;
    wire c_out1, c_out2;
    wire [Narrow-1:0] s_out1;
    wire [Narrow-1:0] s_out2;

```

```

    adder b1(
        .a(A),
        .b(B),
        .c(1'b0),
        .outc(c_out1),
        .outs(s_out1)
    );

```

```

    adder b2(
        .a(A),
        .b(4'b0001),
        .c(1'b0),
        .outc(c_out2),
        .outs(s_out2)
    );

```

```

    always @(*)
    begin
        case(in1)
            3'b000: out1 = A * B;
            3'b001: out1 = {A | B, A ^ B};
            3'b010: out1 = {c_out1, s_out1};
            3'b011: out1 = A + B;
            3'b100: out1 = {c_out2, s_out2};
            3'b101: out1 = |A | B;
            3'b110: out1 = B << A;
            3'b111: out1 = B >> A;
            default: out1 = 8'b0000_0000;
        endcase
    end
endmodule

```

endmodule

```

module adder(a, b, c, outc, outs);
    parameter Narrow = 4;
    input [Narrow-1:0] a;
    input [Narrow-1:0] b;
    input c;
    output outc;
    output [Narrow-1:0] outs;
    wire connect1, connect2, connect3;

```

```

    full_adder e(
        .A(a[0]),
        .B(b[0]),
        .cin(c),
        .S(outs[0]),

```

```

        .cout(connect1)
    );

    full_adder f(
        .A(a[1]),
        .B(b[1]),
        .cin(connect1),
        .S(outs[1]),
        .cout(connect2)
    );

    full_adder g(
        .A(a[2]),
        .B(b[2]),
        .cin(connect2),
        .S(outs[2]),
        .cout(connect3)
    );

    full_adder h(
        .A(a[3]),
        .B(b[3]),
        .cin(connect3),
        .S(outs[3]),
        .cout(outc)
    );
endmodule

module full_adder(A, B, cin, S, cout);
    input A;
    input B;
    input cin;
    output S;
    output cout;

    assign cout = A&B | A&cin | B&cin;
    assign S = A ^ B ^ cin;
endmodule

module hex(in2, in3, in4, in5, o2, o3, o4, o5, o6, o7, o8);
    input in2;
    input in3;
    input in4;
    input in5;
    output o2;
    output o3;
    output o4;
    output o5;
    output o6;
    output o7;
    output o8;

    hex0 u1(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out1(o2)
    );

    hex1 u2(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out2(o3)
    );

    hex2 u3(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out3(o4)
    );

    hex3 u4(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out4(o5)
    );

    hex4 u5(
        .c3(in2),

```

```

        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out5(o6)
    );

    hex5 u6(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out6(o7)
    );

    hex6 u7(
        .c3(in2),
        .c2(in3),
        .c1(in4),
        .c0(in5),
        .out7(o8)
    );
endmodule

module hex0(c3, c2, c1, c0, out1);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out1; //output

    assign out1 = ~c3 & c2 & ~c1 & ~c0 | c3 & c2 & ~c1 & c0 |
    c3 & ~c2 & c1 & c0 | ~c3 & ~c2 & ~c1 & c0;
endmodule

module hex1(c3, c2, c1, c0, out2);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out2; //output

    assign out2 = c2 & c1 & ~c0 | c3 & c1 & c0 | ~c3 & c2 & ~c1
    & c0 | c3 & c2 & ~c0;
endmodule

module hex2(c3, c2, c1, c0, out3);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out3; //output

    assign out3 = ~c3 & ~c2 & c1 & ~c0 | c3 & c2 & c1 | c3 & c2
    & ~c0;
endmodule

module hex3(c3, c2, c1, c0, out4);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out4; //output

    assign out4 = ~c3 & c2 & ~c1 & ~c0 | ~c2 & ~c1 & c0 | c2 &
    c1 & c0 | c3 & ~c2 & c1 & ~c0;
endmodule

module hex4(c3, c2, c1, c0, out5);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;
    output out5; //output

    assign out5 = ~c3 & c2 & ~c1 | ~c2 & ~c1 & c0 | ~c3 & c0;
endmodule

module hex5(c3, c2, c1, c0, out6);
    input c3; //selected when s is 0
    input c2; //selected when s is 1
    input c1; //select signal
    input c0;

```

```

output out6; //output

assign out6 = ~c3 & ~c2 & c0 | ~c3 & ~c2 & c1 | ~c3 & c1 &
c0 | c3 & c2 & ~c1 & c0;

endmodule

module hex6(c3, c2, c1, c0, out7);
input c3; //selected when s is 0

```

```


input c2; //selected when s is 1
input c1; //select signal
input c0;
output out7; //output

assign out7 = ~c3 & ~c2 & ~c1 | c3 & c2 & ~c1 & ~c0 | ~c3 &
c2 & c1 & c0;

endmodule

```

2. Simulation.

 

(this is just a part of all the simulation)


Part III

1. What is the behaviour of the 8-bit shift register shown in Figure 6 when $Load_n = 1$ and

$ShiftRight = 0$?

The output of last time will be the new input, so there would be a recursion that the inout and the output will keep same until $Load_n$ or $ShiftRight$ change.

2. Draw a schematic.

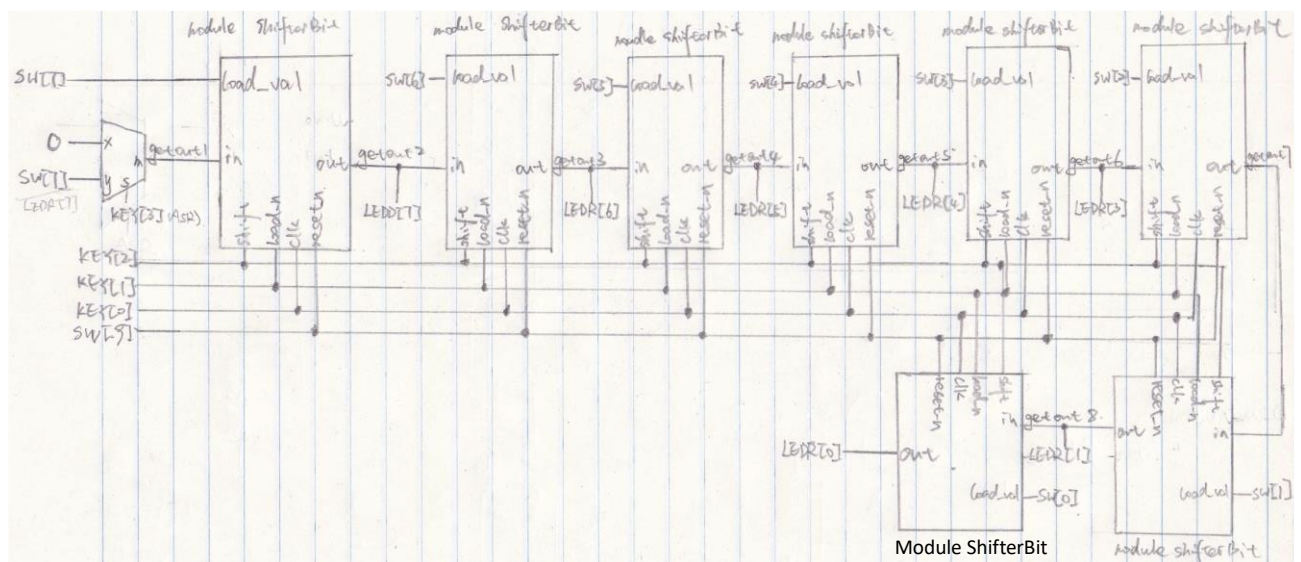

3.4. Write a Verilog.

```
module mux(LED, SW, KEY);
    input [9:0] SW;
    input [3:0] KEY;
    output [9:0] LED;
    wire getout1, getout2, getout3, getout4, getout5, getout6, getout7, getout8;

    mux2to1 M1(
        .x(1'b0),
        .y(LED[7]),
        .s(KEY[3]),
        .m(getout1)
    );

    ShifterBit B1(
        .load_val(SW[7]),
        .in(getout1),
        .shift(KEY[2]),
        .load_n(KEY[1]),
        .clk(KEY[0]),
        .reset_n(SW[9]),
        .out(getout2)
    );

    assign LED[7] = getout2;

    ShifterBit B2(
        .load_val(SW[6]),
        .in(getout2),
        .shift(KEY[2]),
        .load_n(KEY[1]),
        .clk(KEY[0]),
        .reset_n(SW[9]),
        .out(getout3)
    );

    assign LED[6] = getout3;

    ShifterBit B3(
        .load_val(SW[5]),
        .in(getout3),
        .shift(KEY[2]),
        .load_n(KEY[1]),
        .clk(KEY[0]),
        .reset_n(SW[9]),
        .out(getout4)
    );

    assign LED[5] = getout4;

    ShifterBit B4(
        .load_val(SW[4]),
        .in(getout4),
        .shift(KEY[2]),
        .load_n(KEY[1]),
        .clk(KEY[0]),
        .reset_n(SW[9]),
        .out(getout5)
    );

    assign LED[4] = getout5;

    ShifterBit B5(
        .load_val(SW[3]),
        .in(getout5),
        .shift(KEY[2]),
        .load_n(KEY[1]),
        .clk(KEY[0]),
        .reset_n(SW[9]),
        .out(getout6)
    );

    assign LED[3] = getout6;

    ShifterBit B6(
        .load_val(SW[2]),
        .in(getout6),
        .shift(KEY[2]),
        .load_n(KEY[1]),
        .clk(KEY[0]),
        .reset_n(SW[9]),
        .out(getout7)
    );
```

```

    assign LEDR[2] = getout7;

    ShifterBit B7(
        .load_val(SW[1]),
        .in(getout7),
        .shift(KEY[2]),
        .load_n(KEY[1]),
        .clk(KEY[0]),
        .reset_n(SW[9]),
        .out(getout8)
    );

    assign LEDR[1] = getout8;

    ShifterBit B8(
        .load_val(SW[0]),
        .in(getout8),
        .shift(KEY[2]),
        .load_n(KEY[1]),
        .clk(KEY[0]),
        .reset_n(SW[9]),
        .out(LED[0])
    );
endmodule

module ShifterBit(load_val, in, shift, load_n, clk, reset_n, out);
    input load_val, in, shift, load_n, clk, reset_n;
    output out;
    wire connect1, connect2;

    mux2to1 M2(
        .x(out),
        .y(in),
        .s(shift),
        .m(connect1)
    );

    mux2to1 M3(
        .x(load_val),
        .y(connect1),
        .s(load_n),
        .m(connect2)
    );

    D_flipflop D1(
        .d(connect2),
        .clock(clk),
        .reset_n(reset_n),
        .q(out)
    );
endmodule

module mux2to1(x, y, s, m);
    input x; //selected when s is 0
    input y; //selected when s is 1
    input s; //select signal
    output m; //output

    assign m = s & y | ~s & x;
endmodule

module D_flipflop(d, clock, reset_n, q);
    parameter N = 1;
    input [N-1:0] d;
    input [N-1:0] clock;
    input [N-1:0] reset_n;
    output [N-1:0] q;
    reg [N-1:0] q;

    always @(posedge clock)
    begin
        if (reset_n == 1'b0)
            q <= 0;
        else
            q <= d;
        end
    end
endmodule

```

5. Simulation.

